

## Lab 6: RC Circuits

Zachary Pouska  
001103193

Natalie Tran  
000698629

PHYS 236 | Fall 2022  
Date performed: 11/02/2022

## 1 Purpose

## 2 Theory

## 3 Experiment Analysis

$$V_c = \varepsilon \left(1 - e^{-\frac{t}{\tau}}\right) | \div$$

## 4 Procedure

## 5 Data and Graphs

### 5.1 Part I: Calculate the value of the time constant

The measured value of capacitance of the the capacitor is **104.7 $\mu$ F**

The measured value of the resistor using the DMM is **0.987M $\Omega$**

#### Calculated Time Constants

$\tau_{measured}$ (sec)	$\tau_{nominal}$ (sec)	% Error
103.34	100	3.34





## 5.2 Part II: Charging the capacitor

**Voltage v Time for Charging**

Time (sec)	Voltage (V)
5	0.198
10	0.361
15	0.494
20	0.626
25	0.757
30	0.868
35	0.993
40	1.087
45	1.189
50	1.287
55	1.375
60	1.455
65	1.549
70	1.617
75	1.698
80	1.772
85	1.832
90	1.9
100	2.033
110	2.136
120	2.245
130	2.343
140	2.43
150	2.514
160	2.594
170	2.667
185	2.767
200	2.855
220	2.956
240	3.047
260	3.125
280	3.193
305	3.265
330	3.328
355	3.375
380	3.419
400	3.449
420	3.473
435	3.491
450	3.507
465	3.519
480	3.535
500	3.548
510	3.556
540	3.575
570	3.589
630	3.612
720	3.634
780	3.648

**Voltage v Time Linearized**


Time (sec)	$-\frac{1}{\tau}$
5	-0.051
10	-0.094
15	0.148
20	0.191
25	0.236
30	0.276
35	0.323
40	0.359
45	0.401
50	0.442
55	0.481
60	0.518
65	0.563
70	0.596
75	0.638
80	0.678
85	0.711
90	0.750
100	0.832
110	0.900
120	0.977
130	1.052
140	1.124
150	1.198
160	1.275
170	1.350
185	1.464
200	1.575
220	1.721
240	1.873
260	2.025
280	2.180
305	2.375
330	2.583
355	2.773
380	2.990
400	3.171
420	3.345
435	3.497
450	3.656
465	3.794
480	4.014

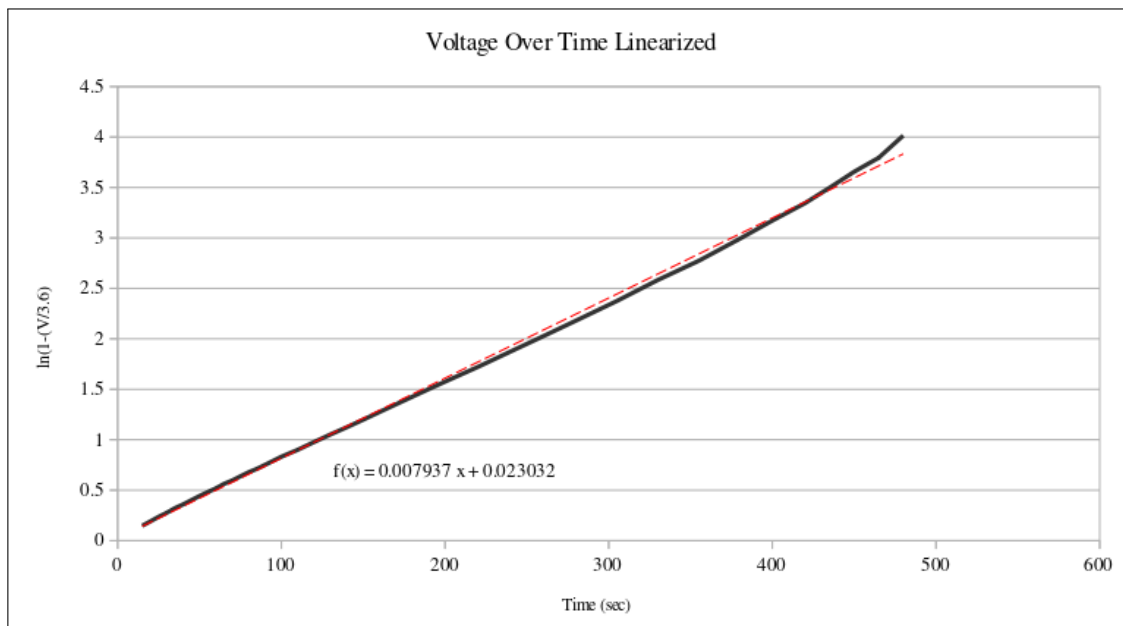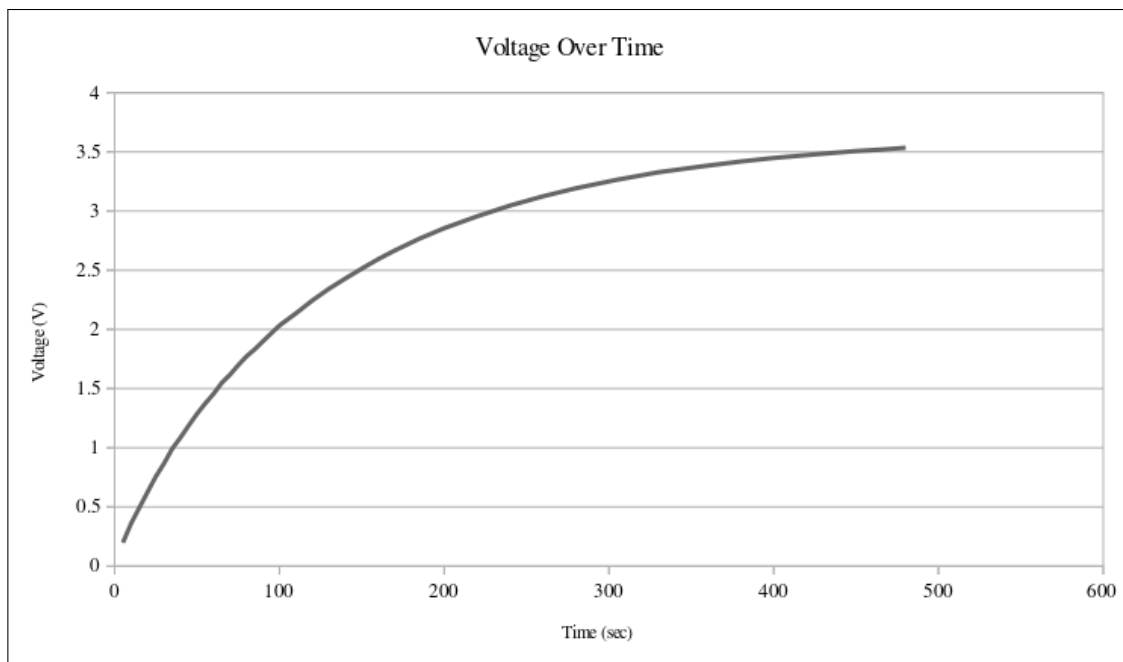

### 5.3 Part III: Discharging the capacitor

Voltage v Time for Discharging

Time (sec)	Voltage (V)
5	0.198
10	0.361
15	0.494
20	0.626
25	0.757
30	0.868
35	0.993
40	1.087
45	1.189
50	1.287
55	1.375
60	1.455
65	1.549
70	1.617
75	1.698
80	1.772
85	1.832
90	1.9
100	2.033
110	2.136
120	2.245
130	2.343
140	2.43
150	2.514
160	2.594
170	2.667
185	2.767
200	2.855
220	2.956
240	3.047
260	3.125
280	3.193
305	3.265
330	3.328
355	3.375
380	3.419
400	3.449
420	3.473
435	3.491
450	3.507
465	3.519
480	3.535

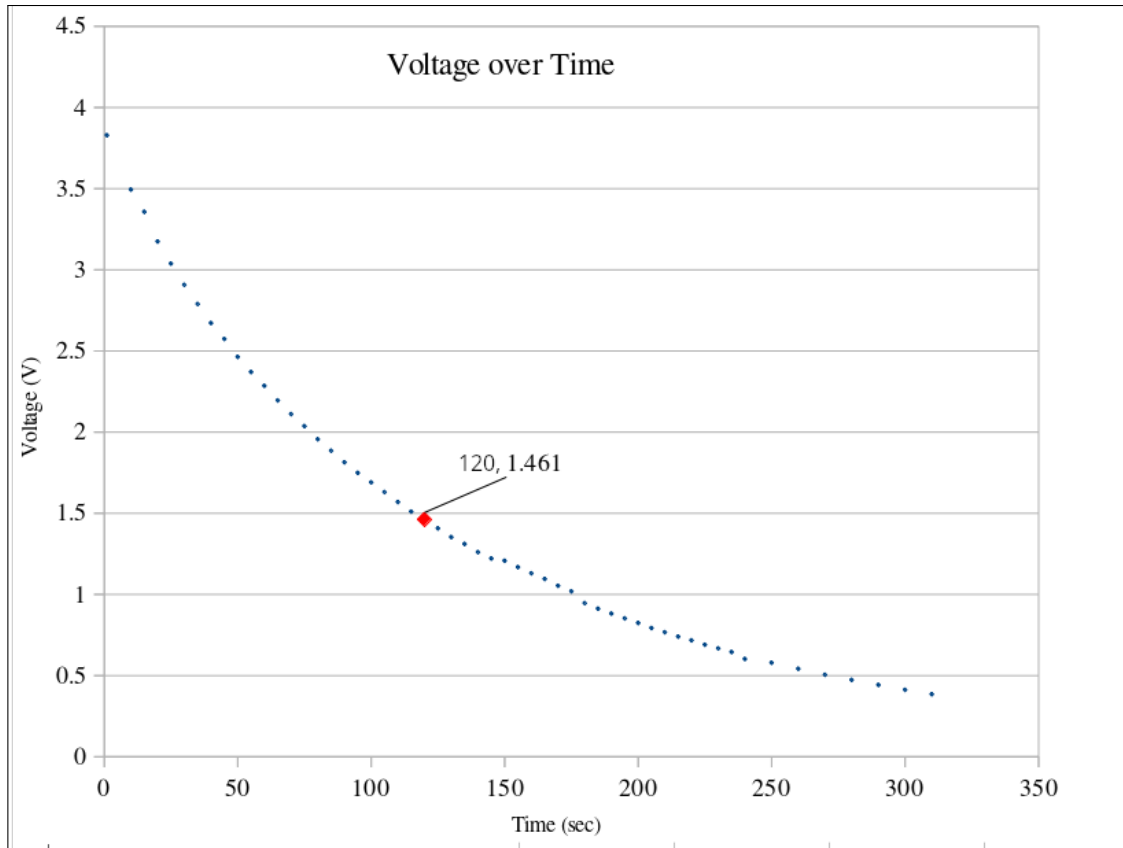

## 5.4 Part IV: Connecting R and C in parallel

The voltage read across the resistor with the DMM is **4.009 V**

The voltage read across the capacitor with the DMM is **4.009 V**

# 6 Results

## 6.1 Part I: Calculate the value of the time constant

To calculate the time constant ( $\tau$ ) the resistor is multiplied by the capacitor value via the equation

$$\tau = RC$$

Substitute the measured values of resistance and capacitance in the equation to retrieve the data values stated in Section 5.1.

To calculate the percent error between the expected time constant vs actual time constant created from differing expected resistance and capacitance values, the percent error formula is used

$$\%error = \frac{|\tau_{measured} - \tau_{nominal}|}{\tau_{nominal}} \times 100$$

## 6.2 Part II: Charging the capacitor

In order to linearize the voltage values measured, the following expression is examined:

$$V_c = \varepsilon \left( 1 - e^{-\frac{t}{\tau}} \right)$$

### 6.3 Part III: Discharging the capacitor

The time constant can be determined by selecting the value of voltage in which it is 37% of the max voltage (emf). Then, at that point, the time is the time constant.  $0.37 \times 4.0V = 1.48$ . The closest point to 1.48 in our graph is 1.461, in which the time is 120 seconds. This means the determined time constant from discharging is 120.

### 6.4 Part IV: Connecting R and C in parallel

To calculate the current through the resistor, the equation  $V = IR$  is used. Manipulating this equation, current can be found via  $I = V/R$ . Using the measured values of resistance and voltage, current can be found as  $\frac{4.009V}{0.987M\Omega} = 4.062\mu A$ .

The max charge can be calculated using the equation  $Q_{max} = C\varepsilon$  substituting values,  $104.7\mu F \times 4.009V = 419.7\mu C$ . The energy stored in the capacitor can be found using the equation  $U = \frac{1}{2}C\varepsilon^2$ . Substituting values,  $\frac{1}{2}104.7\mu F \times 4.009^2 = 841.4\mu J$

## 7 Questions

### 7.1 Part 4

1. Do you obtain the same values for the voltage across the resistor and capacitor? Explain.  
**Yes! They are in parallel, so the potential difference across each should be the same. If the potential difference wasn't equal, that wouldn't make sense, as measuring the potential difference across each one is essentially connecting the multimeter to the same point in the circuit, assuming 0 resistance in the wires.**
2. Is the current across the resistor zero? Explain.  
**No. In the case of the resistor and capacitor being in series, as the capacitor fills up, it blocks the current flow through the resistor. In this configuration, as the capacitor charges more current is simply diverted through the resistor instead of through the capacitor.**

## 8 Conclusion