

## Lab 6: RC Circuits

Zachary Pouska  
001103193

Natalie Tran  
000698629

PHYS 236 | Fall 2022  
Date performed: 11/02/2022

## 1 Purpose

## 2 Theory

## 3 Experiment Analysis

$$V_c = \varepsilon \left(1 - e^{-\frac{t}{\tau}}\right) | \div$$

## 4 Procedure

## 5 Data and Graphs

### 5.1 Part 1

### 5.2 Part 2

### 5.3 Part 3

## 6 Results

## 7 Questions

### 7.1 Part 1

### 7.2 Part 2

### 7.3 Part 3

### 7.4 Part 4

1. Do you obtain the same values for the voltage across the resistor and capacitor? Explain.  
**Yes! They are in parallel, so the potential difference across each should be the same. If the potential difference wasn't equal, that wouldn't make sense, as measuring the potential difference across each one is essentially connecting the multimeter to the same point in the circuit, assuming 0 resistance in the wires.**
2. Is the current across the resistor zero? Explain.  
**No. In the case of the resistor and capacitor being in series, as the capacitor fills up, it blocks the current flow through the resistor. In this configuration, as the capacitor charges more current is simply diverted through the resistor instead of through the capacitor.**

## 8 Conclusion